

The logo for EDICON 2018, featuring the text "EDI" in a blue box above "CON" in a white box with a blue border.

2018

Electronic Design Innovation  
Conference & Exhibition

The event details: "October 17-19 2018", "Santa Clara Convention Center", and "Santa Clara, CA".


# Power Distribution Network (PDN) Impedance and Target Impedance

Steve Sandler, Picotest

Eric Bogatin, Teledyne LeCroy


Larry Smith, [PDNPowerIntegrity.com](http://PDNPowerIntegrity.com)

# A Typical PDN

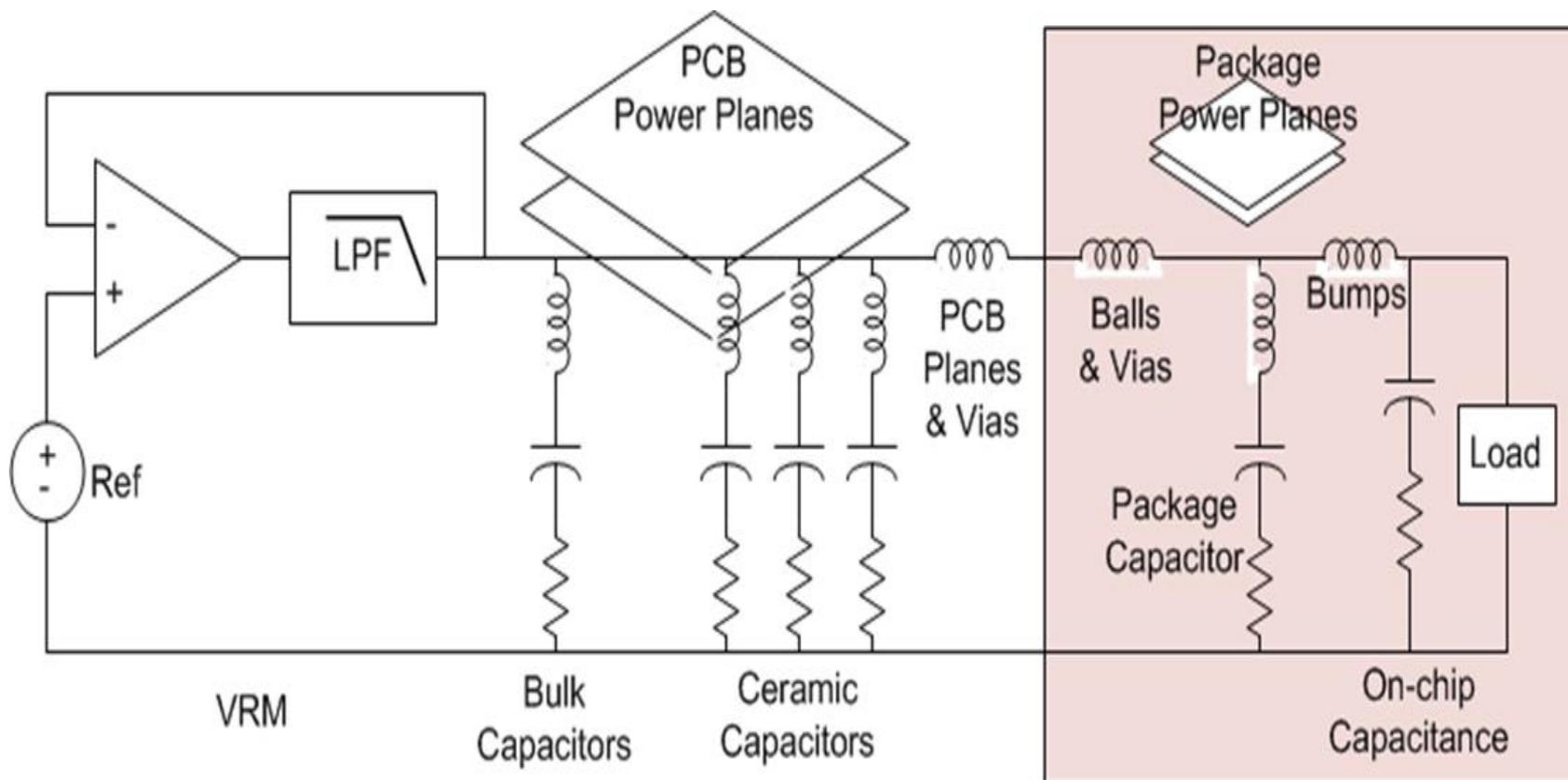


# Power Integrity


Is about managing  
noise voltage here

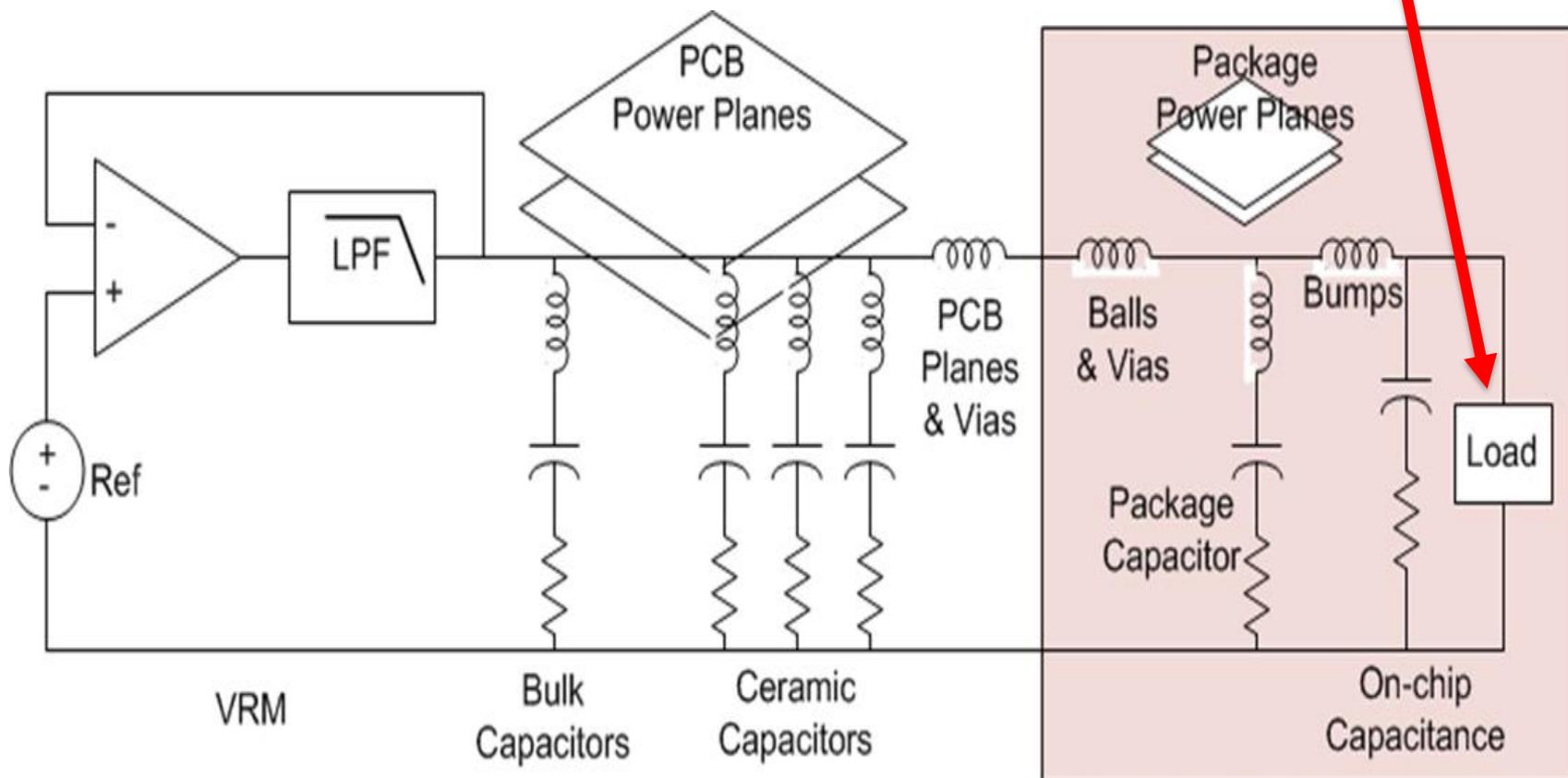

# Dual(ing) Noise Sources

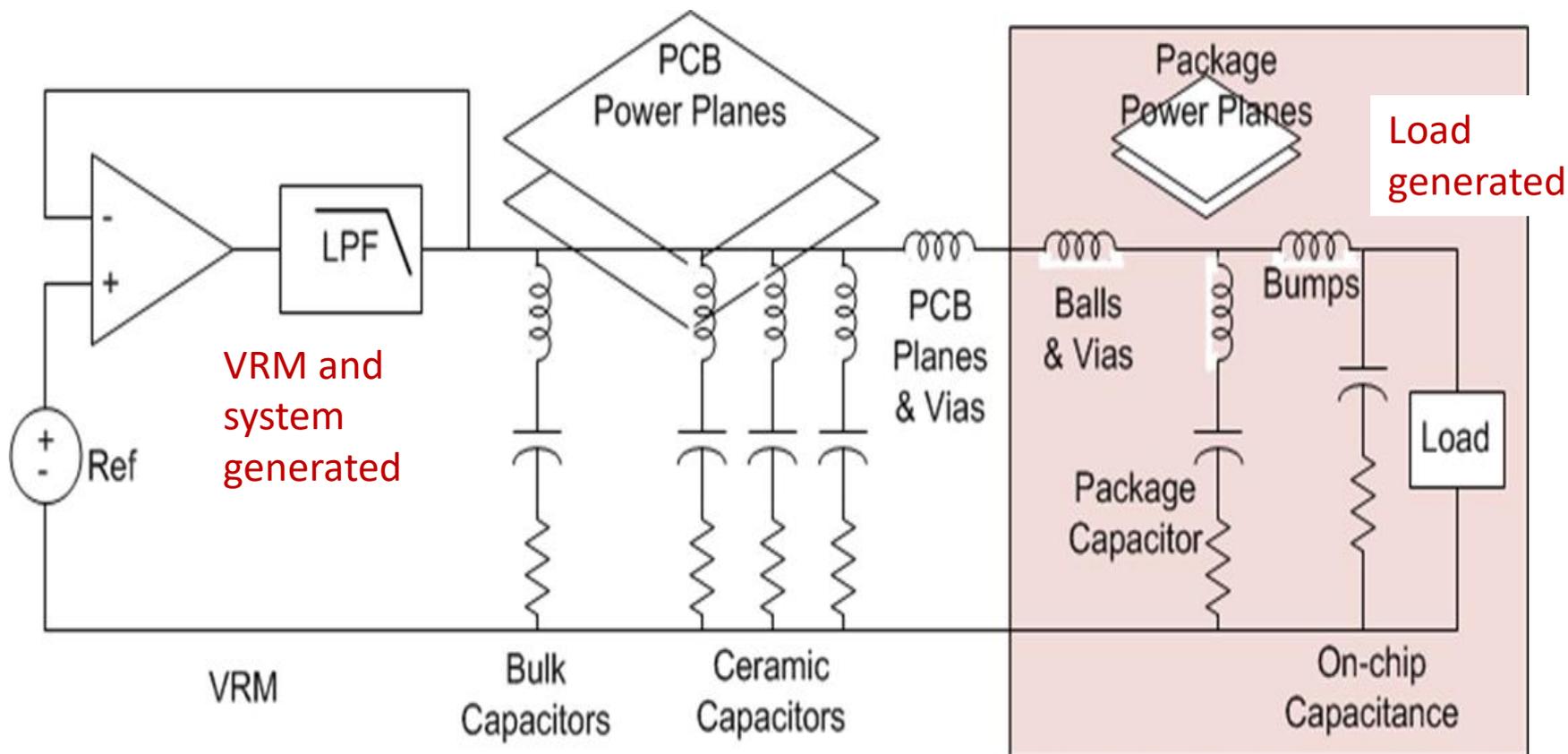


# Flat Impedance is Ideal, but...

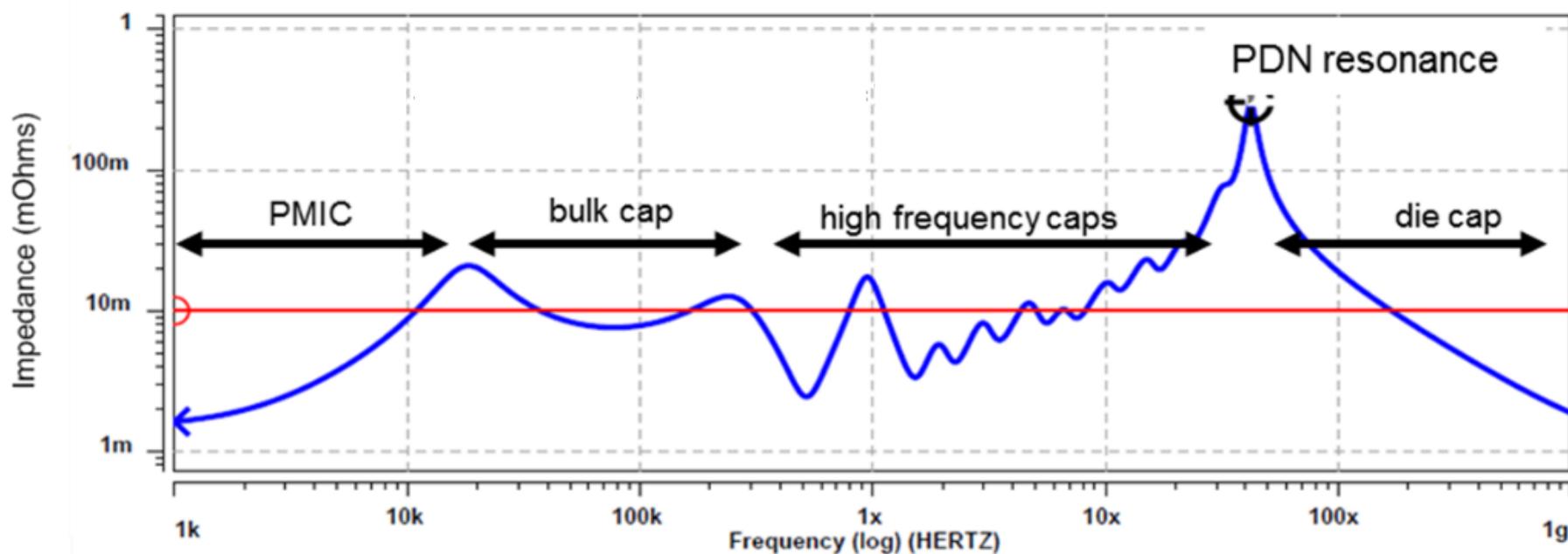

Impedance ignores the VRM generated noise

# The Nature of a Peak

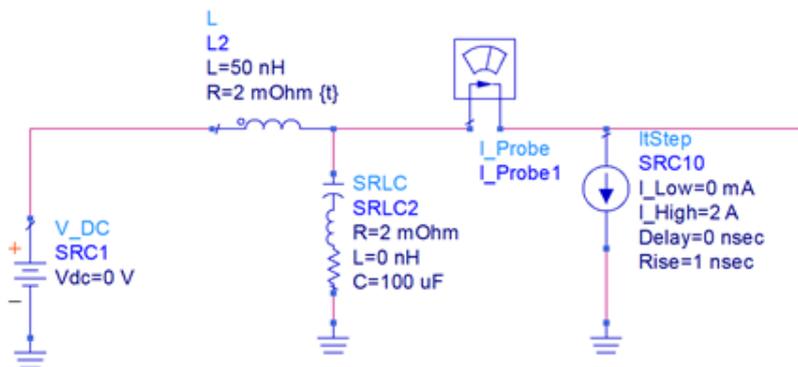


Single resonant circuit with a “target impedance” of 125mΩ is used to demonstrate the voltage response to a fixed dynamic current amplitude

$$Z_o = \sqrt{\frac{L}{C}} = \sqrt{\frac{50nH}{100uF}} = 22.4m\Omega$$

$$Q = \frac{Z_o}{R} = \frac{22.4m\Omega}{4m\Omega} = 5.6$$

$$Z_{pk} = Z_o \cdot Q = 125m\Omega$$

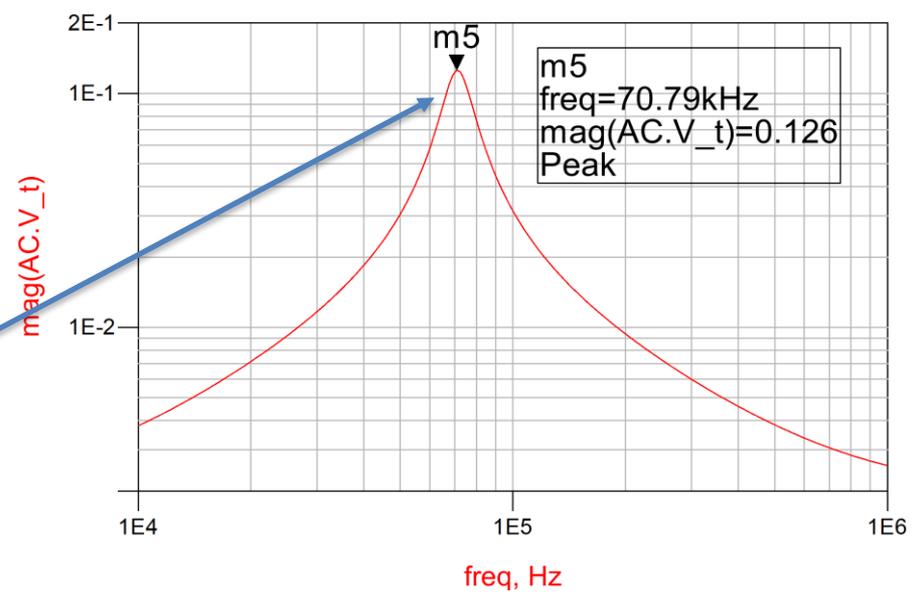

### Natural Response


## STEP PROFILE

Laplace provides the time domain response

$$V(s) = \frac{1}{C} \cdot \frac{\Delta I}{\frac{1}{RC}s + \frac{1}{LC} + s^2}$$

Exponential decay
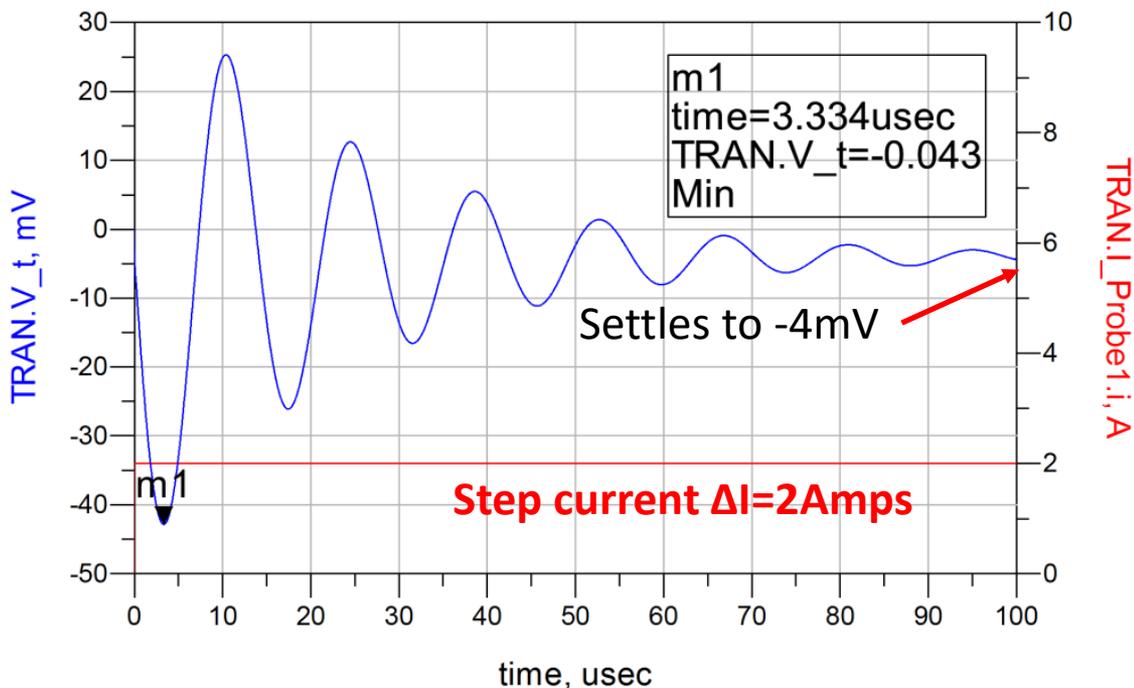
$$V(t) = \frac{\Delta I}{C \cdot \sqrt{\omega_0^2 - \alpha^2}} \cdot e^{-\alpha t} \cdot \sin \sqrt{(\omega_0^2 - \alpha^2) t}$$



$$|\Delta V| = 43\text{mVpk}$$

### RESONANT SINE

Exponential growth


$$V(s) = \Delta I \cdot Q \cdot \sqrt{\frac{L}{C}} \cdot \left[ \sin(\omega_o) \cdot t - e^{-\frac{\omega_o}{2Q}t} \cdot \sin\left(\sqrt{\omega_o^2 - \frac{\omega_o^2}{2Q}}\right) t \right]$$

Note: Q is now in the numerator

Forced Response

$|\Delta V| = 124\text{mVpk}$

Sine current  $\Delta I = 2\text{Amps}$

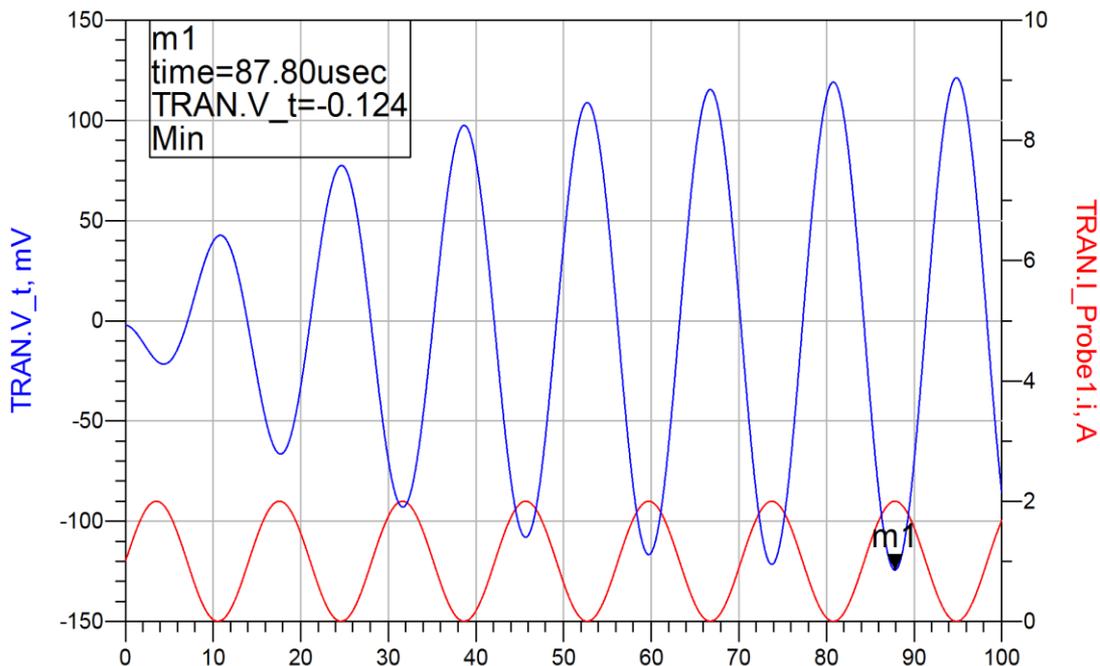

# RESONANT SQUARE

27% larger than sine excitation

The Fourier transform of a square wave at any harmonic, n


$$\frac{2}{T} \left[ \int_0^{n\pi} A \cdot \sin(nt) dt + \int_{n\pi}^{2n\pi} A \cdot \sin(nt) dt \right] = \frac{4}{n\pi} = \frac{1.273}{n}$$

$$\frac{4 \cdot 124mV}{\pi} = 158mVpk$$

$|\Delta V| = 158mVpk$

Square current  $\Delta I = 2Amps$

## Forced Response

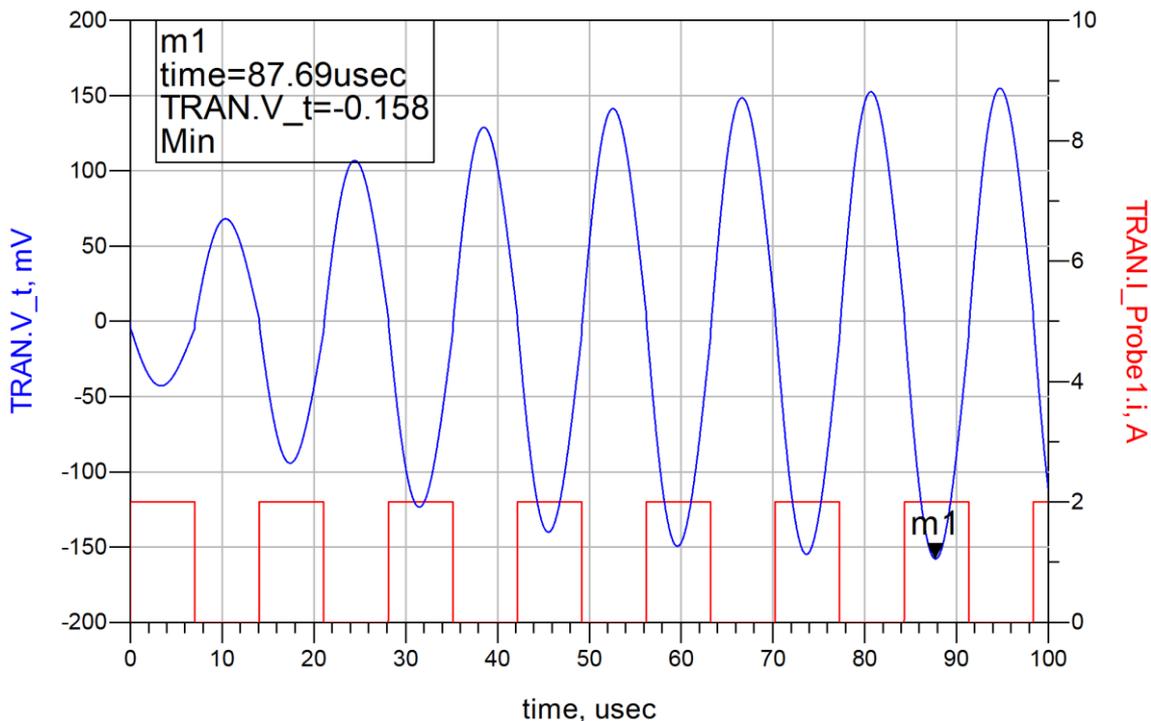


# The Two response

This oscilloscope screenshot shows both the natural (step) response and the forced (resonant square wave) response at the same time.

The exponential decay, exponential growth and impact of resonant  $Q$  are all clear here.




## Multiple Resonances

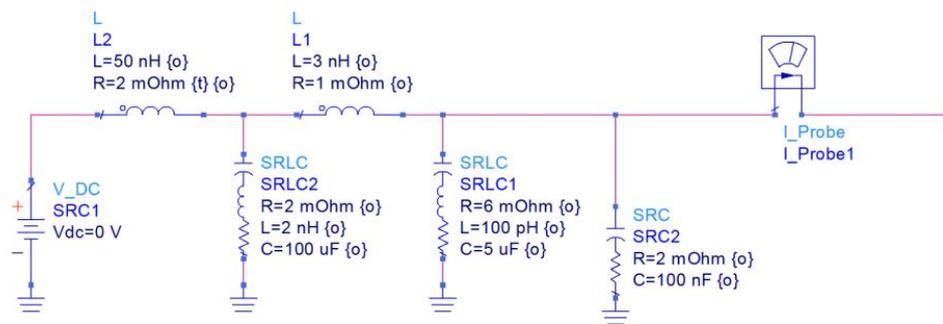

Three resonances, each with a peak impedance of 125mΩ

What will the excursion be for a  $\Delta I$  of 2A?

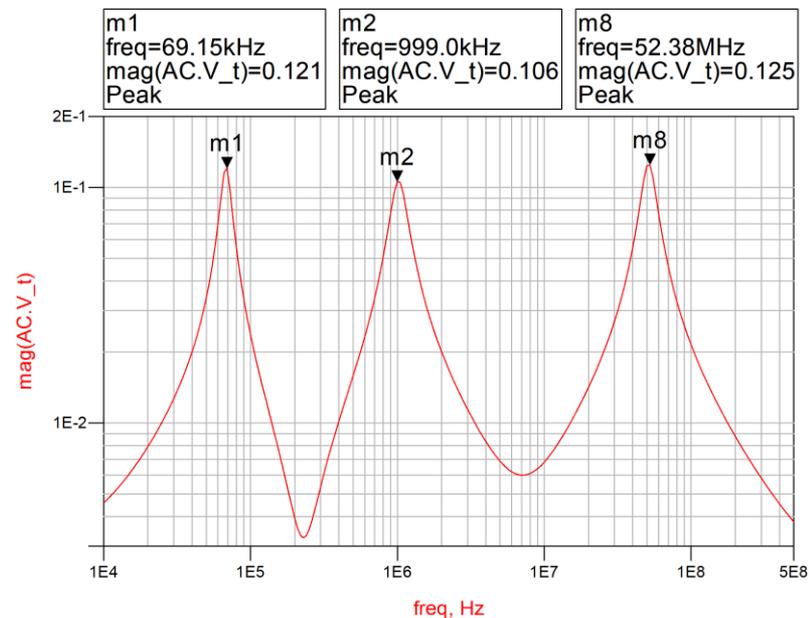Most PDNs exhibit more than one resonant peak







# Rogue Waves

Creating a worst case current pattern results in a voltage response of 586mVpk.

The excursions were all excited and phased to sum – resulting in a Rogue wave.

This is more than 10X the response to a single 125mΩ peak step response.
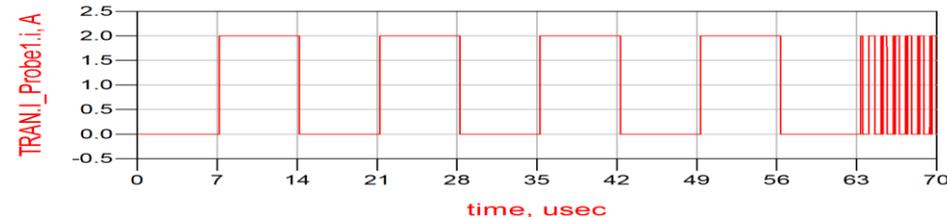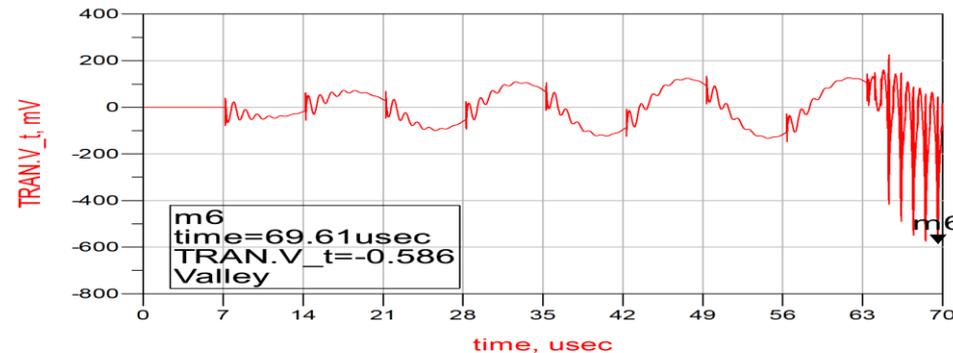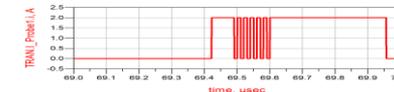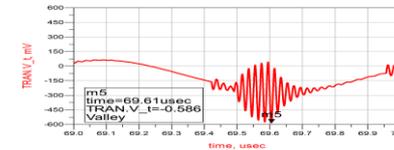
$$\Delta V_{rogue} \approx \Delta I \sum_0^n Z_i$$



# Target Impedance

For a single Impedance peak

$$V_{pk-pk} = I_{pk-pk} \cdot \frac{4 \cdot Z_{pk}}{\pi}$$

Solving for an equivalent impedance

$$Z_{target} = \frac{V_{pk-pk}}{I_{pk-pk}} \cdot \frac{\pi}{4}$$

Target Impedance Bandwidth

$$Z_{BW} = \frac{0.35}{t_{edge}}$$


But beware of additional resonances and noise sources!

# Dynamic Current is Complicated

When the core activity starts it appears as both a step and also as high frequency content

When the activity stops it appears as a step.

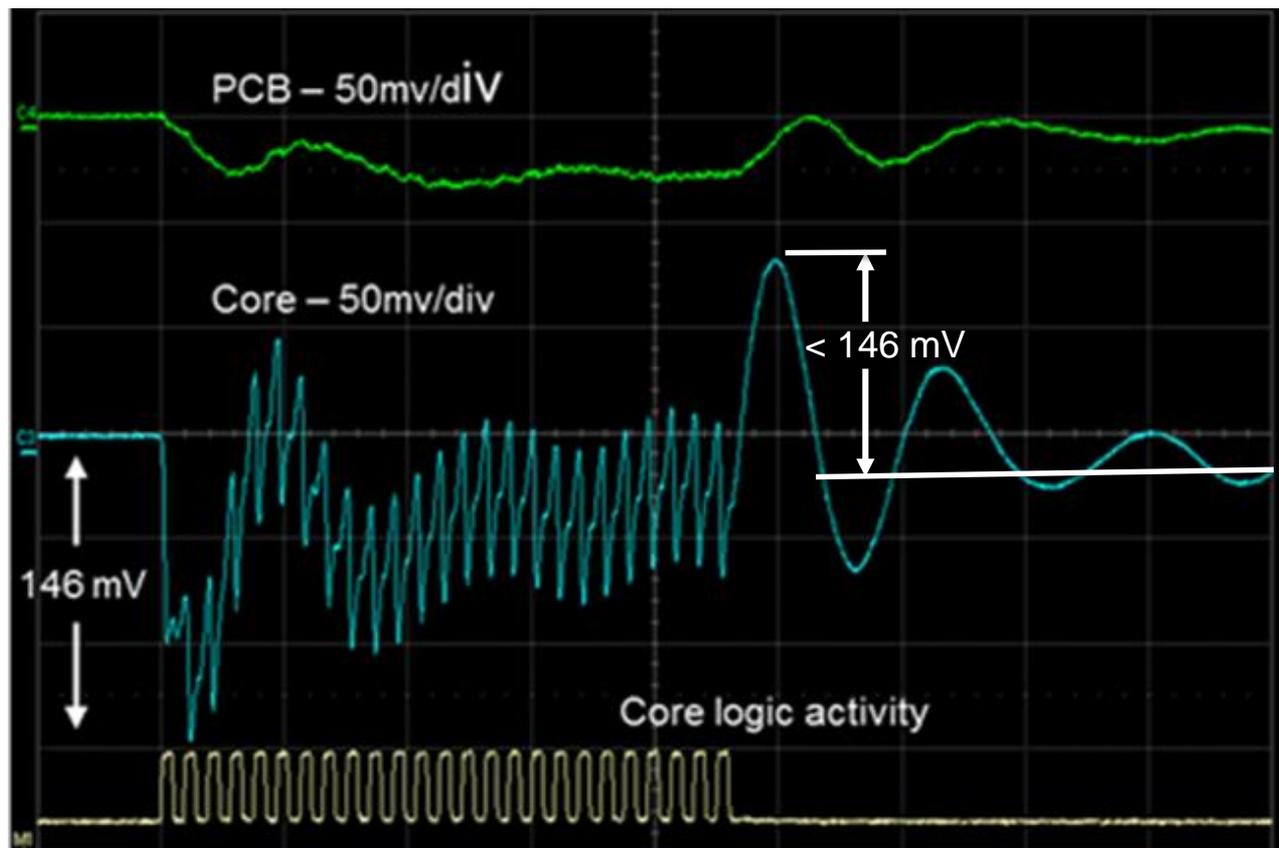
The exponential decay is clear and the response is asymmetric


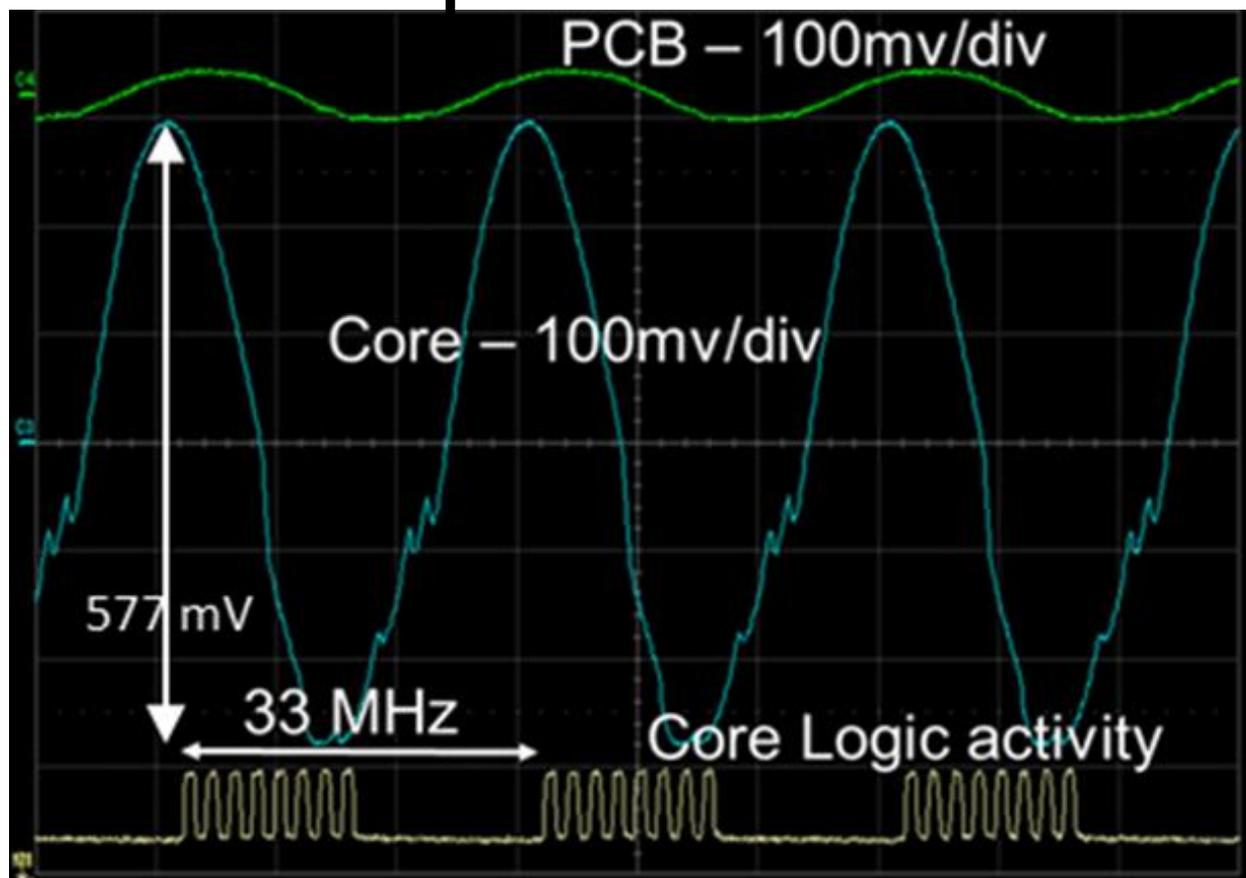
# Forced Response

When the core activity is at a repetition rate that matches the die resonant peak, we can see the much larger forced response.


We can't see the exponential growth in this picture


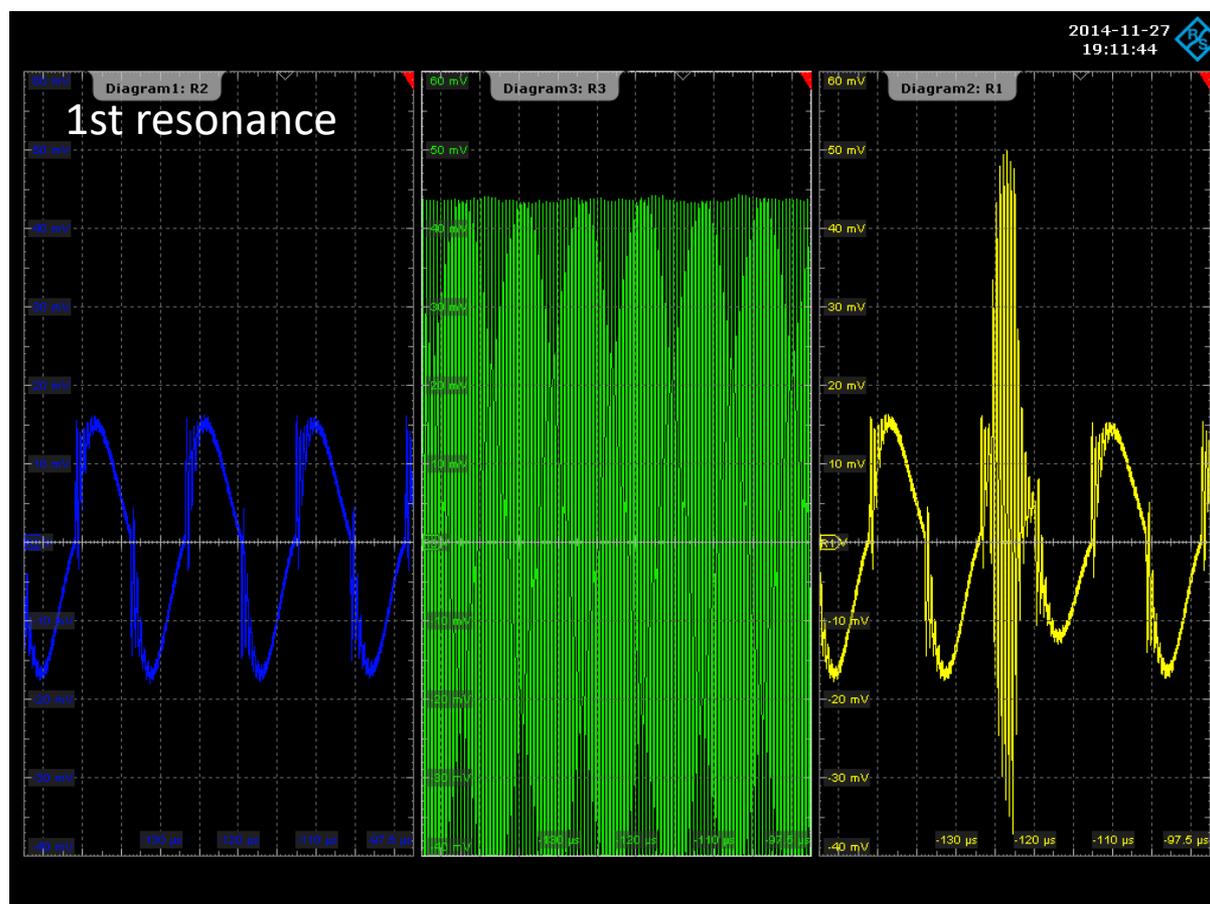
# Rogue Wave

Rogue waves may be rare, but do exist and are relatively simple to generate in the lab.

This oscilloscope screen shot shows a Rogue wave on the output of a DDR termination regulator.





2018

Electronic Design Innovation  
Conference & Exhibition

October 17-19 2018  
Santa Clara Convention Center  
Santa Clara, CA

# Conclusions

1. Target impedance is a tool that helps design a robust PDN that results in acceptable noise
2. While flat impedance is ideal, careful management of the peaks can result in an acceptable design
3. Keep in mind that the VRM and system also generate noise that will appear at the die
4. Multiple sources are additive.



# Thanks for Attending Our Session!

Maintain your Integrity - Power Responsibly

## REFERENCES

1. Larry D. Smith, Eric Bogatin, “Principles of Power Integrity for PDN Design--Simplified: Robust and Cost Effective Design for High Speed Digital Products” (Prentice Hall Modern Semiconductor Design), ISBN-13: 978-0132735551, April 6, 2017
2. Sandler, S, “Power Integrity: Measuring, Optimizing, and Troubleshooting Power Related Parameters in Electronics Systems”, Nov 18, 2014
3. W. Cheng, A. Sarkar, S. Lin, and Z. Zheng, “Worst case switching pattern for core noise analysis,” DesignCon, 2009.
4. S. Sun, L. D. Smith, and P. Boyle, “On-chip PDN noise characterization and modeling,” DesignCon, 2010.
5. L. D. Smith, S. Sun, P. Boyle, and B. Krsnik, "System power distribution network theory and performance with various noise current stimuli including impacts on chip level timing," in *Proc. Custom Integrated Circuits Conference*, San Jose, CA, 2009.
6. I. Novak, “Comparison of power distribution network design methods: Bypass capacitor selection based on time domain and frequency domain performances”. Manuscript for TF-MP3 “Comparison of Power Distribution Network Design Methods” at DesignCon 2006, February 6-9, 2006, Santa Clara, CA
7. C. K. Cheng “Power Distribution Network Simulation and Analysis” UCSD March, 4, 2010
8. Hu, Xiang, Peng Du, and Chung-Kuan Cheng. "Exploring the rogue wave phenomenon in 3D power distribution networks." *Electrical Performance of Electronic Packaging and Systems (EPEPS)*, 2010 IEEE 19th Conference on. IEEE, 2010.